

Thumbs Rule: Main problem of TRF-Rx is insufficient adjacent frequency rejection (poor adjacent signal rejection). This is mainly due to large BW and low Q of the selectivity curve.

Another serious problem of TRF-Rx is that Q curve shape varies over the tuning range.

Q.8 What is the Ganged tuned circuit in the Rxs?

LECTURE # 28 (STARTS HERE)

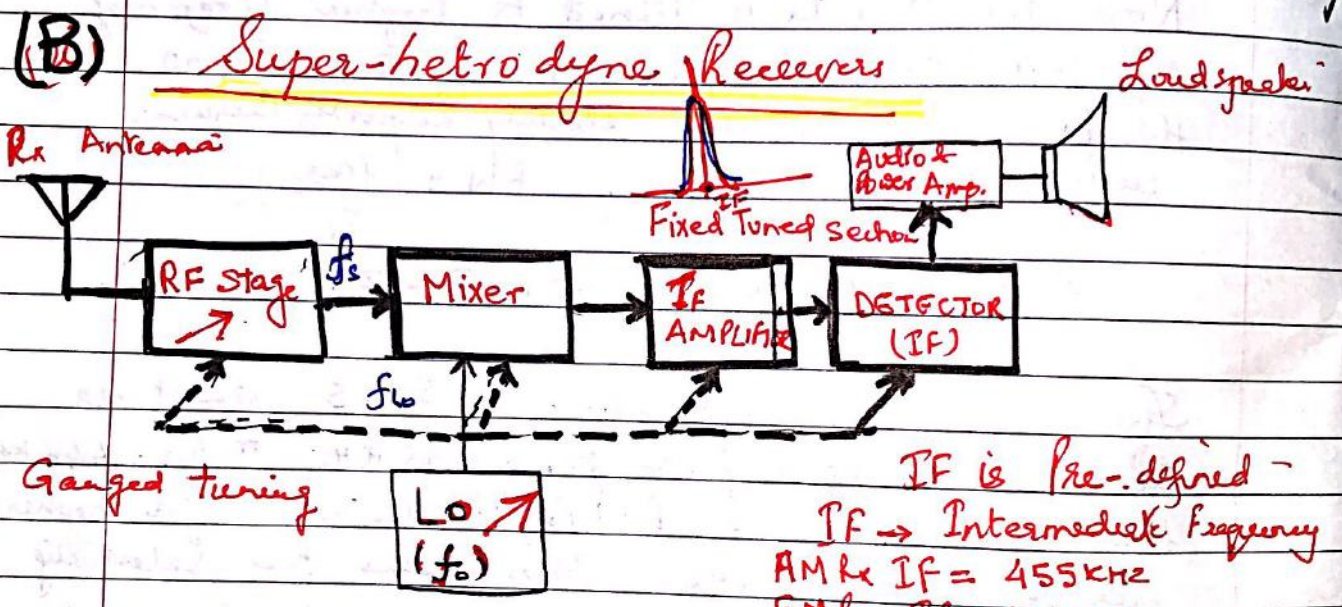


Figure 14 Block Diagram of a Superheterodyne Rx.

The above figure no 14 shows a basic Super-heterodyne Rx block diagram. This is the basic practical version. Other versions are also available. Superheterodyne is used in radio and TV Rxs. This technique allows the Rxs to be tuned to a particular IF (intermediate frequency) even though the front end is variably tuned. This implies

that front end of Super-heterodyne is Variably tuned to any of the desired modulated carriers just like the TRF Rx. However the intermediate stage is fixed tuned to a particular IF only. To explain this statement further let us assume the incoming carrier frequency range is  $f_{c_1} = 535 \text{ kHz}$  to  $1640 \text{ kHz}$ . This means that lowest modulated carrier expected at antenna is  $535 \text{ kHz}$  and the highest modulated carrier at Rx antenna is  $1640 \text{ kHz}$ . So the front end can be Variably tuned from  $535 \text{ kHz}$  to  $1640 \text{ kHz}$ . Now, according to Super-heterodyne technique the middle stage of Rx will always be fixed tuned to a particular IF no matter where the front end is tuned to. For any front-end tuning position range  $535 \text{ kHz} - 1640 \text{ kHz}$ , the middle stage is always fixed tuned to IF.

### Purpose of using IF (intermediate Frequency):

In typical Amplitude Modulation (AM Radio) in US the receivers use  $\text{IF} = 455 \text{ kHz}$ .

IF for FM Rx, it is usually  $= 10.7 \text{ MHz}$

IF for Television is  $= 45 \text{ MHz}$ .

In any of the above cases, the IF stage is so designed so that the Amplifiers are highly selective to the IF. Subsequent stages following the IF amplifier are also designed to perform best around this IF. From this we realize that just as in TRF-Rx here also in Super-heterodyne Rx the front end shows BW variation,  $Q$  variation and response curve variation, & Selectivity variation over the tuning range. But this demerit is overcome by the middle IF stage which is

designed to offer best selectivity & response curve.

### Three principal parts of a Super-hetrodyne

The three principal parts of a Superhetrodyne are

- (i) Local Oscillator ( $f_{LO}$ )
- (ii) Mixer
- (iii) IF amplifier

Before we can explain further, we write the brief introduction of each of these three parts.

Local Oscillator :- This produces a signal ( $f_{LO}$ ) close to the signal to be detected.

It is preferred that if  $f_{s-min}$  denotes the minimum tuning position (eg 535 kHz) then  $f_{LO} < f_{s-min}$ .

Mixer : This performs mixing operation b/w two inputs - (i) The modulated carrier ( $f_s$ ) and (ii) the local oscillator ( $f_{LO}$ ). With these inputs fed to this non-linear device will produce outputs like  $f_s$ ,  $f_{LO}$ ,  $|f_{LO} - f_s|$ ,  $f_s + f_{LO}$ .

$|f_{LO} - f_s|$  implies that if  $f_{LO} > f_s$  then the difference is given as  $f_{LO} - f_s$  but if  $f_{LO} < f_s$  then the difference is  $f_s - f_{LO}$ . Out of all these output components, the difference is the pre-defined

IF. ie  $|f_{LO} - f_s| = IF$


IF Amplifier The subsequent stage is the IF amplifier which is designed so that its

$$f_{res} = IF = |f_{LO} - f_s|$$

The Q curve of the IF amp has high selective, narrow bandwidth curve so that this resonance curve will cancel and attenuate all the components  $f_s, f_{LO}, f_{LO} + f_s$  but will pass without attenuation if  $f_{res} = IF = |f_{LO} - f_s|$
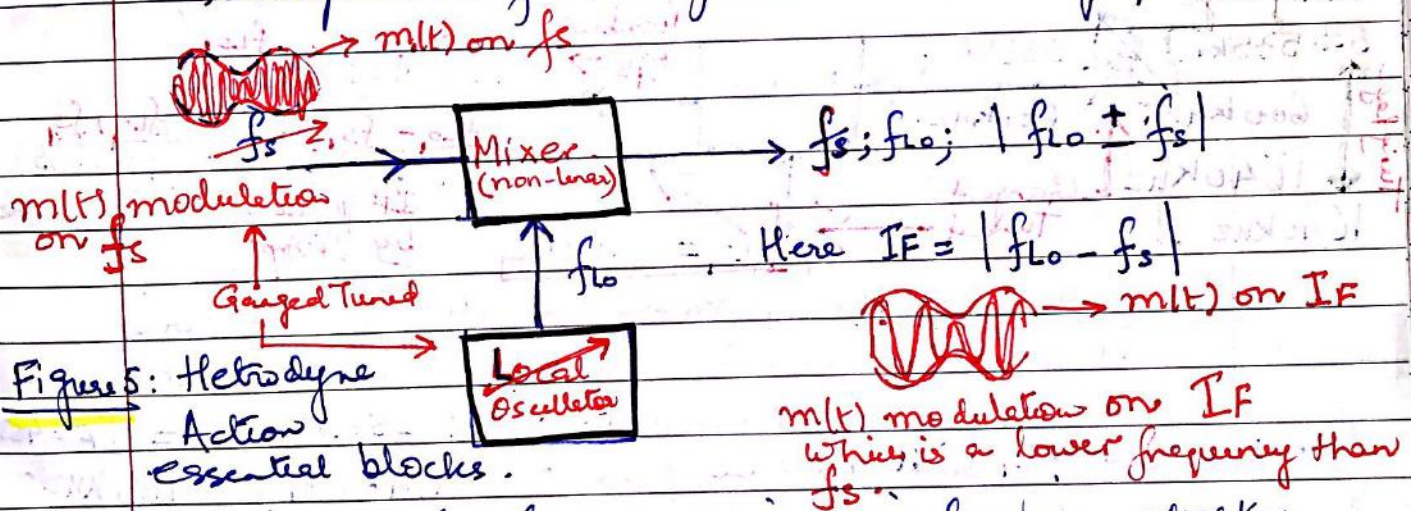
### Heterodyne Action of Local Oscillator, Mixer & IF Amplifier

Super-heterodyne action used in Radio and TV Rxs is a technique that allows the Rxs to be always fixed tuned to a particular pre-defined IF irrespective of the front end tuning position.



Already it has been explained in previous chapters that the mixer is a non-linear device. It is basically an amplitude modulator which will be a result of mixing action between inputs  $f_s$  &  $f_{LO}$ . Due to the amplitude modulation action of a Mixer the output will be mainly 3 components  $\rightarrow |f_{LO} - f_s|, f_{LO}, (f_{LO} + f_s)$  as is expected in case of an amplitude modulator. However  $f_s$  also trickles down through the mixer and appears at output some modulation as  $f_s$  now appears on IF too.

## Examples of Super-Heterodyne Action..

Case (a) If  $f_{LO} > f_s$  then  $IF = f_{LO} - f_s$ , where  $f_{LO}$  is the local oscillator frequency.  
Down Conversion  $IF = 455 \text{ kHz}$

$IF = |f_{LO} - f_s|$  or  $f_{LO} = IF + f_s$

This means the local oscillator is designed to oscillate at such a frequency so that difference of  $f_{LO}$  &  $f_s$  always produces IF

IMP In case of Down Conversion,  $f_{LO} > f_s$ ;  $IF = f_{LO} - f_s$ ;  $f_s > IF$

Example (i) Let  $f_s = 535 \text{ kHz}$  &  $IF = 455 \text{ kHz}$


Then  $f_{LO} = IF + f_s$

$= (455 + 535) \text{ kHz}$

$f_{LO} = 990 \text{ kHz}$

Figure no 6

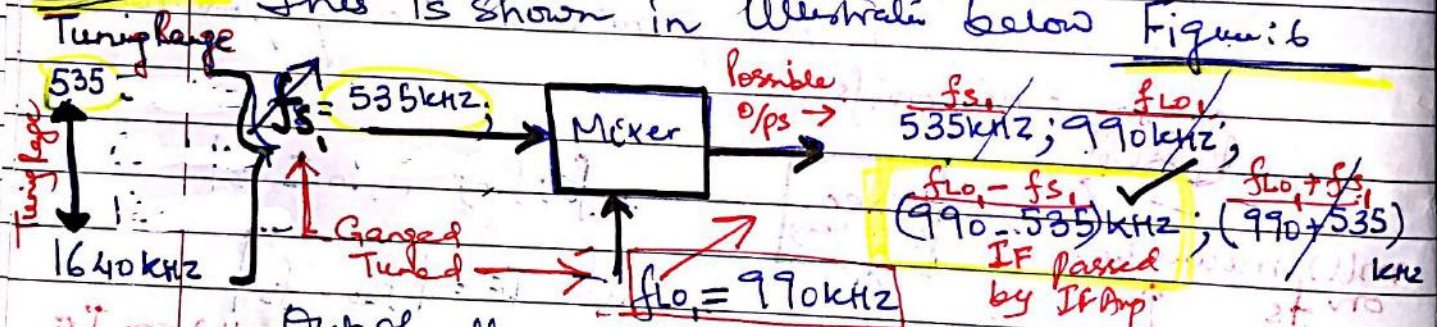This is shown in block diagram below Figure 6



Out of all the possible outputs the following IF amplifier carries all the components but its  $f_{res}$  matches with  $(990 - 535) \text{ kHz} = IF = 455$  kHz. Modulation on  $f_s$  will now be present on  $(f_s - f_{LO}) = 455 \text{ kHz}$

Example (ii) Now let us tune to next station say at  $f_{s2} = 600 \text{ kHz}$ .

$f_s$  at  $600 \text{ kHz}$  is  $65 \text{ kHz}$  above first station position of  $f_s$  at  $535 \text{ kHz}$ .

IMP → A very important point to note in case of Superheterodyne action is that the local oscillator output also shifts up by  $65 \text{ kHz}$ . The set up is called Ganged Tuning. Due to this Ganged tuning of front end tuner and the local oscillator, now  $f_{LO} = 990 \text{ kHz} + 65 \text{ kHz}$ . ∴ New LO oscillates for second tuning position is

Given as  $f_{LO2} = f_{LO1} + 65 \text{ kHz} = 1055 \text{ kHz}$

IMP  $\rightarrow$  This again implies that a mixing action takes place between  $f_{s2} = 600 \text{ kHz}$  and  $f_{LO2} = 1055 \text{ kHz}$  to produce following possible outputs at the mixer o/p:

Mixer o/p in second tuning position =  $f_{s2}, f_{LO2}, |f_{LO2} - f_{s2}|, f_{LO2} + f_{s2}$   
 $= 600 \text{ kHz}; 1055 \text{ kHz}; 455 \text{ kHz}; 1655 \text{ kHz}$

$\rightarrow$  IF Passed by IF Amp.

Hence out of all these components at o/p of mixer the subsequent IF Amp with same  $f_{IF} = 455 \text{ kHz}$  cancels all other components but allows to pass only  $455 \text{ kHz}$ . Here also the modulation (information) on  $f_{s2} = 600 \text{ kHz}$  will also be present on  $f_{IF} = (f_{LO2} - f_{s2}) = 455 \text{ kHz}$ .

Example (iii) Like wise let us tune to the highest position on the tuning range. Here  $f_{s3}$  at  $1640 \text{ kHz}$  which is  $1040 \text{ kHz}$  above previous tuning position  $f_{s2}$  at  $600 \text{ kHz}$ . Due to Ganged Tuning the Capacitor in  $L_0$  also changes to produce  $f_{LO3} = f_{LO2} + 1040 \text{ kHz}$

Now  $L_0$  oscillated at  $f_{LO3} = 1055 \text{ kHz} + 1040 \text{ kHz} = 2095 \text{ kHz}$

This again implies that a mixing action takes place between  $f_{s3} = 1640 \text{ kHz}$  and  $f_{LO3} = 2095 \text{ kHz}$  to produce following possible output at mixer o/p:

Mixer o/p in third tuning position =  $f_{s3}; f_{LO3}; |f_{LO3} - f_{s3}|, f_{LO3} + f_{s3}$   
 $= 1640 \text{ kHz}; 2095 \text{ kHz}; 455 \text{ kHz}; 3735 \text{ kHz}$

$\rightarrow$  IF Passed thro IF Amp.

Wherever the modulation information is on  $f_{s3}$  will also be present on  $(f_{LO3} - f_{s3}) = 455 \text{ kHz}$ .

CONTD: IMPORTANT POINTS OF SUPERHETERODYNE RX.

Imp → Earlier modulation (m(t)) before mixing operation, was carried by  $f_s$ . After mixing operation, the modulation (m(t)) will be carried by all those components in which  $f_s$  appears. These are  $f_s$  itself,  $f_{lo} - f_s$ , and  $f_{lo} + f_s$ .

Imp. Down Conversion Defn. When  $f_s > IF$ ;  $f_{lo} > f_s$   
Since modulation (m(t)) was carried by  $f_s$  prior to mixing operation and after mixing operation modulation (m(t)) is carried on the selected predefined IF where  $f_s > IF$ . Then this is called Down Conversion.  
e.g as in example (i)  $f_{s1} = 535 \text{ kHz} > 455 \text{ kHz}$ ;  $f_{lo1} = 990 \text{ kHz}$   
example (ii)  $f_{s2} = 600 \text{ kHz} > 455 \text{ kHz}$ ;  $f_{lo2} = 1055$   
example (iii)  $f_{s3} = 1640 \text{ kHz} > 455 \text{ kHz}$ ;  $f_{lo3} = 2095$

In other words modulation is now carried on a lower frequency, hence this is called down conversion.

Imp:- Now we can say output is an IF modulated signal.

Imp The superheterodyne Rx. offers a ganged arrangement of capacitors where all the capacitors are ganged tuned. Any change in one capacitor results in a corresponding change in the other capacitors. It is due to this ganged arrangement that as  $f_s$  changes, so does  $f_{lo}$  to maintain  $\omega_p$  mixer always as IF as one of the components.

→ Another possibility of Down Conversion (so that  $f_s > IF$ ) is when  $f_{LO} < f_s$ ; so that  $IF = f_s - f_{LO}$ .


Case (b) If  $f_{LO} < f_s$  then  $IF = f_s - f_{LO}$  where predefined  $IF = 455 kHz$ .  
Down Conversion  $IF = |f_{LO} - f_s|$ ;  $f_s > f_{LO}$ , Here also  $f_s > IF$ .  
However here  $IF = f_s - f_{LO}$

Example IV :- Let  $f_{s1} = 535 kHz$  &  $IF = 455 kHz$ .  
then in this case of down conversion  
since  $f_{s1} > f_{LO}$   $\therefore IF = f_{s1} - f_{LO}$ .

This implies  $455 kHz = 535 kHz - f_{LO}$ .

$\therefore$  Required  $f_{LO} = 535 kHz - 455 kHz = 80 kHz$   
Here also  $f_{s1}$  gets down converted to  $IF$  where  $f_{s1} > IF$ , however here we are now using  $L_O (f_{LO})$  frequency smaller than  $f_{s1}$ .  
This is shown in illustration no Figure 7 below:

Figure no: 7

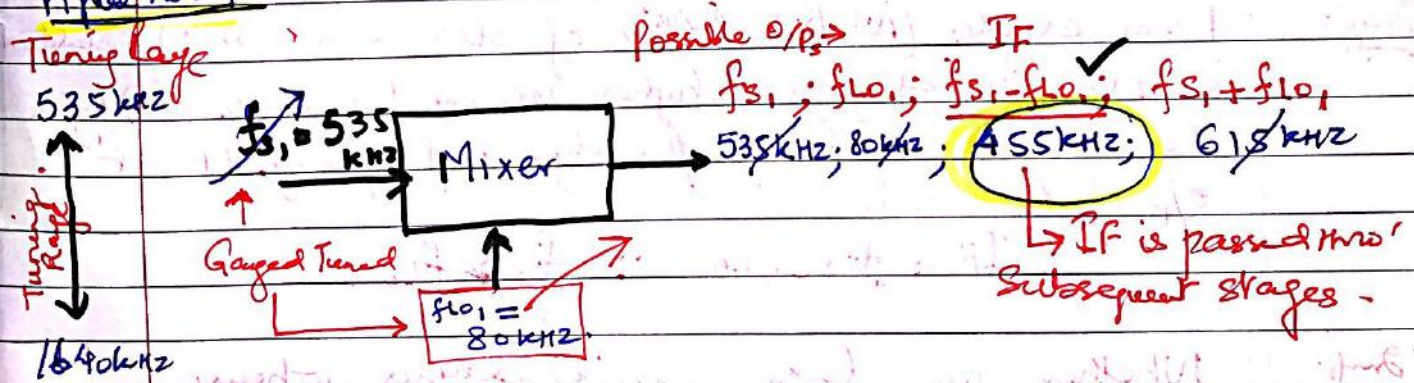

Example V Let  $f_{s2} = 700 kHz$ , &  $IF = 455 kHz$ ; Then  $IF = f_{s2} - f_{LO2}$   
 $\therefore f_{LO2} = f_{s2} - IF \Rightarrow f_{LO2} = 700 kHz - 455 kHz$   
 $\therefore f_{LO2} = 245 kHz$ .

Example VI: Let  $f_{s3} = 1640 kHz$  &  $IF = 455 kHz$ , Then  $IF = f_{s3} - f_{LO3}$   
 $\therefore f_{LO3} = f_{s3} - IF \Rightarrow f_{LO3} = 1640 kHz - 455 kHz$   
 $\therefore f_{LO3} = 1,185 kHz$



Imp:-

In the following Down converted cases as explained in examples (iv), (v) & (vi), we summarize the study as a Down converted defn where

$f_s > IF$ ;  $f_{LO} < f_s$ ; &  $IF = f_s - f_{LO}$

Here also before mixing the mlt) baseband modulation is carried on a higher frequency  $f_s$  and after mixing the same modulation is now translated on a lower IF frequency. where

- Example (iv)  $f_{s1} = 535 \text{ kHz} > 455 \text{ kHz}$ ;  $f_{LO1} = 80 \text{ kHz}$
- Example (v)  $f_{s2} = 700 \text{ kHz} > 455 \text{ kHz}$ ;  $f_{LO2} = 245 \text{ kHz}$
- Example (vi)  $f_{s3} = 1640 \text{ kHz} > 455 \text{ kHz}$ ;  $f_{LO3} = 1185 \text{ kHz}$

Imp:-

From examples (i), (ii) & (iii) of down conversion, mlt) modulat is shifted from a higher frequency ( $f_s$ ) to a lower pre-defined frequency IF at opp of  $f_c$  where

$IF = f_{LO} - f_s \quad \because f_{LO} > f_s$

Case (b)

Imp:-

From examples (iv), (v) & (vi) of down conversion, mlt) modulation is also shifted from a higher incoming frequency ( $f_s$ ) before the mixer to a lower pre-defined frequency IF at opp of  $f_c$  where

$IF = f_s - f_{LO} \quad \because f_s > f_{LO}$


Imp:-

Whether we take Case (a) examples where  $IF = f_{LO} - f_s$  or Case (b) examples where  $IF = f_s - f_{LO}$ ; in either cases every incremental change in the tuning position of  $f_s$  results in an equal incremental changes in  $f_{LO}$  values also. This is possible only because the capacitive element in front end tuner and capacitive element in LO are ganged together. This is called Ganged tuning.

Down Conversion + Up Conversion (Contd.)Case (c) Up Conversion

If  $IF = f_s + f_{LO}$ , this implies that  $f_s = IF - f_{LO}$  and  $f_s < IF$ . Here modulation (mt) is carried on a lower frequency ( $f_s$ ) before mixing operation and after mixed operation it is carried on a higher frequency  $IF$ . This would be referred to as Upconversion. See figure no. 8.

Figure no. 8

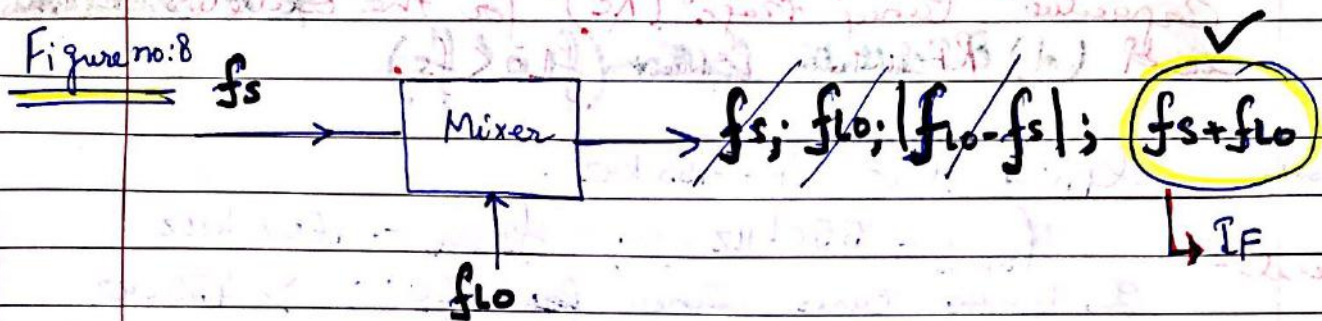

Imp:-

Q.9

In Superhetrodyne Rx. out of the many possible o/p's of the mixer (ie  $f_s$ ,  $f_{LO}$ ,  $|f_{LO} - f_s|$ ,  $f_s + f_{LO}$ ) down conversion setup is preferred to upconversion. Thus it would be preferred to have an arrangement where always  $f_s > IF$  so that  $IF = |f_{LO} - f_s|$ . Upconversion arrangement where  $IF = f_{LO} + f_s$  is not preferred. (Why?)

Imp:-

Q.10

Further in downconversion  $f_{LO} > f_s$  is preferred so that  $IF = f_{LO} - f_s$ . (Why?)

Imp:-

Q.11

For the upconversion arrangement the tuning range of 535 kHz - 1640 kHz would not be applicable - (Why?) if  $IF = 455$  kHz.

- Q. 12 A rx is designed to tune to incoming signal carrier frequencies over range  $f_{smin} = 550 \text{ kHz}$  to  $f_{smax} = 1600 \text{ kHz}$ . Assume the predefined  $IF = 445 \text{ kHz}$ .
- (i) Find the frequency tuning range ( $K_f$ ) and the Capacitive tuning range ( $K_c$ ) for the (a) RF section and (b) Oscillator section ( $f_{LO} > f_s$ )
- (ii) Find the frequency tuning range ( $K_f$ ) and the Capacitive tuning range ( $K_c$ ) for the (c) RF section and (d) Oscillator section ( $f_{LO} < f_s$ )

Solution:- Given that  $IF = 445 \text{ kHz}$ .

General:-  $f_{smin} = 550 \text{ kHz}$  ;  $f_{smax} = 1600 \text{ kHz}$ .

In both cases since  $f_{smin} > 445 \text{ kHz}$  and  $f_{smax} > 445 \text{ kHz}$  ( $f_s > IF$ ) therefore this is Superhetrodyne action employing down conversion

Defn  $K_f$ : By Definition Frequency tuning range ( $K_f$ ) is given by  $K_f = \frac{f_{smax}}{f_{smin}}$  and correspondingly

Defn  $K_c$   $K_c$  Capacitive tuning range is obtained from  $K_f$  by using equation substitution of  $f = \frac{1}{2\pi\sqrt{LC}}$ . Hence

$$f_{smax} = \frac{1}{2\pi\sqrt{LC_{min}}}$$

$$f_{smin} = \frac{1}{2\pi\sqrt{LC_{max}}}$$

$$K_c = \frac{C_{max}}{C_{min}} = K_f^2$$

i(a) For  $f_{LO} > f_s$   $\therefore IF = f_{LO} - f_s$ .

RF section is before mixer.

Here  $K_f = \frac{f_{smax}}{f_{smin}} = \frac{1600 \text{ kHz}}{550 \text{ kHz}} = 2.909$

$K_c = K_f^2 = 8.4622 = C_{max}/C_{min} \therefore C_{max} = 8.46 C_{min}$

This implies that to tune from  $f_{smin}$  of  $550 \text{ kHz}$  to  $f_{smax}$  of  $1600 \text{ kHz}$ , Capacitor has to be varied as  $C_{max} = 8.46$  times  $C_{min}$ .

i(b) For the Oscillator Section in case of  $f_{LO} > f_s$  &  $IF = f_{LO} - f_s \therefore f_{LO} = IF + f_s$

$\therefore f_{LO_{min}} = IF + f_{s_{min}} = 455 + 550 = 1005 \text{ kHz}$

$f_{LO_{max}} = IF + f_{s_{max}} = 455 + 1600 = 2055 \text{ kHz}$

Frequency Tuning Range at Oscillator

$R_{f_{LO}} = \frac{f_{LO_{max}}}{f_{LO_{min}}} = \frac{2055 \text{ kHz}}{1005 \text{ kHz}} = 2.045 \text{ kHz}$

This means the oscillator has to change its oscillation from  $f_{LO_{min}} = 1005 \text{ kHz}$  to  $f_{LO_{max}} = 2055 \text{ kHz}$ . To achieve this it has to employ a variable capacitor with the capacitance tuning range of oscillator as  $R_{C_0} = (R_{f_{LO}})^2$

$\therefore R_{C_0} = (2.045)^2 = 4.182 = \frac{C_{O_{max}}}{C_{O_{min}}}$

Therefore required is a variable capacitor at oscillator where  $C_{O_{max}} = 4.182 \cdot C_{O_{min}}$

Q.12

ii(a) Here  $f_{LO} < f_s$ ;  $IF = f_s - f_{LO} \therefore f_{LO} = f_s - IF$

RF Section: Show that here also  $R_f = \frac{f_{s_{max}}}{f_{s_{min}}} = 2.909$

Q.12 Show that correspondingly  $R_C = (R_f)^2 = \frac{C_{max}}{C_{min}} = 8.46$  (Just as in ii(a)).

iii(b) Q.12 Show that in the oscillator section  $R_{f_0} = 12.052$  when  $f_{LO} < f_s$ .

Q.12 Show then in the oscillator section  $R_{C_0} = 144$  when  $f_{LO} < f_s$ .

Important Comment:- With referen to the previous solved example  
 $f_{LO} > f_s$  we conclude that if  $f_{LO} > f_s$ , then tuning  
 range of oscillator with ~~requires~~ capacitive element  
 such that  $C_{max} = 8.46 C_{min}$ .

For RF section requires a variable capacitor so that  
 $C_{max} = 8.46 C_{min}$

For oscillator section requires a variable capacitor so that

$$C_{max} = 4.182 C_{min} \checkmark$$

This is a fractional tuning range of a capacitor

$f_{LO} < f_s$  Here for RF section, we require a variable capacitor  
 of same capacitive tuning range such that  
 $C_{max} = 8.46 C_{min}$

For oscillator section it requires a variable capacitor  
 so that  $C_{max} = 144 C_{min}$

This is not a fractional tuning range of a capacitor

2.p:- Finally we conclude that in case of down conversion  
 Q.10 where  $IF = |f_{LO} - f_s|$ , it is preferred to  
 have  $f_{LO} > f_s$  and not  $f_s > f_{LO}$ . (Why?)